

Using Superposition Principle and Edge Current Model to Compute Impedance of Coil in Logging Tool

Tina Zhao, Gerald Minerbo, John Hunka, Gary Hazen

Schlumberger, 110 Schlumberger Drive, Sugar Land, TX 77478, USA


*tzhao@slb.com

- **Introduction to antenna configuration**

- **COMSOL model building**
 - **Edge model for self impedance R,L**
 - **Alternating TX-RX for self inductance**
 - **Superposition for AC resistance correction**
 - **Stray C computation**


Antenna under study

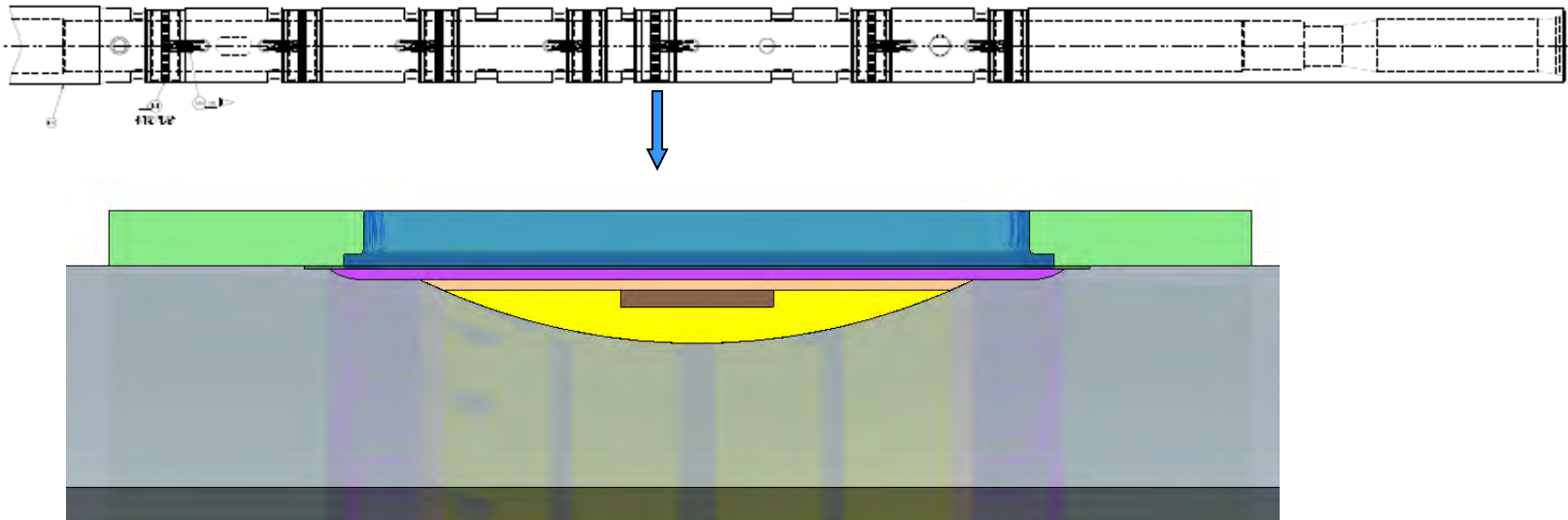- Resistivity logging tool consists of antenna array, and it has 5 transmitters and 2 receivers (T,T,T,R,R,T,T).



- Grey: collar, steel;
- Blue: shield, steel;
- Yellow and orange: fiberglass composite
- Brown: coil wire


How to Build Edge Model to compute Z11

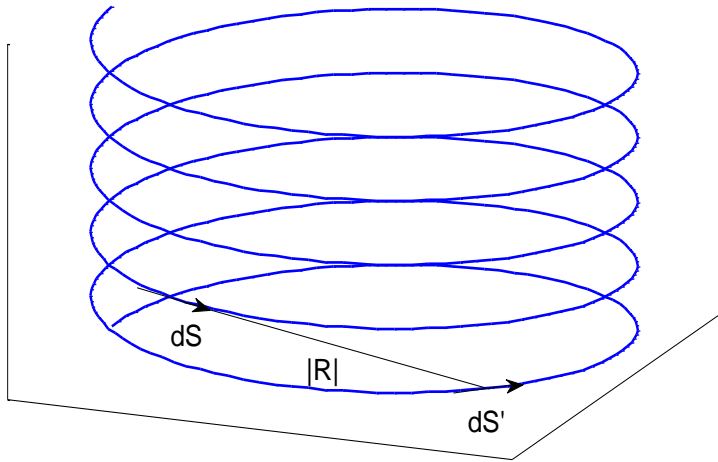

- Neumann formula for low frequency:


$$L = \frac{\mu}{4\pi} \int_C \int_{C'} dS \cdot dS' / |R|$$

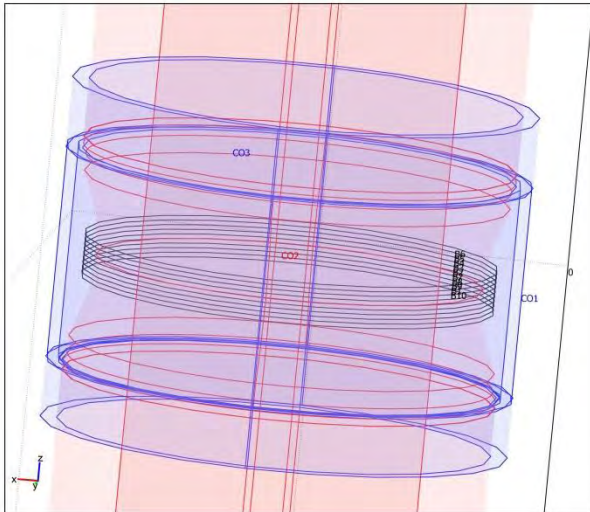- For AWG 18($d=1\text{mm}$), skin depth is 0.1mm and 0.046mm at 400 kHz and 2 MHz.
- R can be zero for self inductance computation
- Analytical solution for coil in air is available, but not for with 3D collar and shield
- Difficult to mesh for thin wire at high frequency
- Use Edge to model thin wire with small skin depth



3D structure around coil

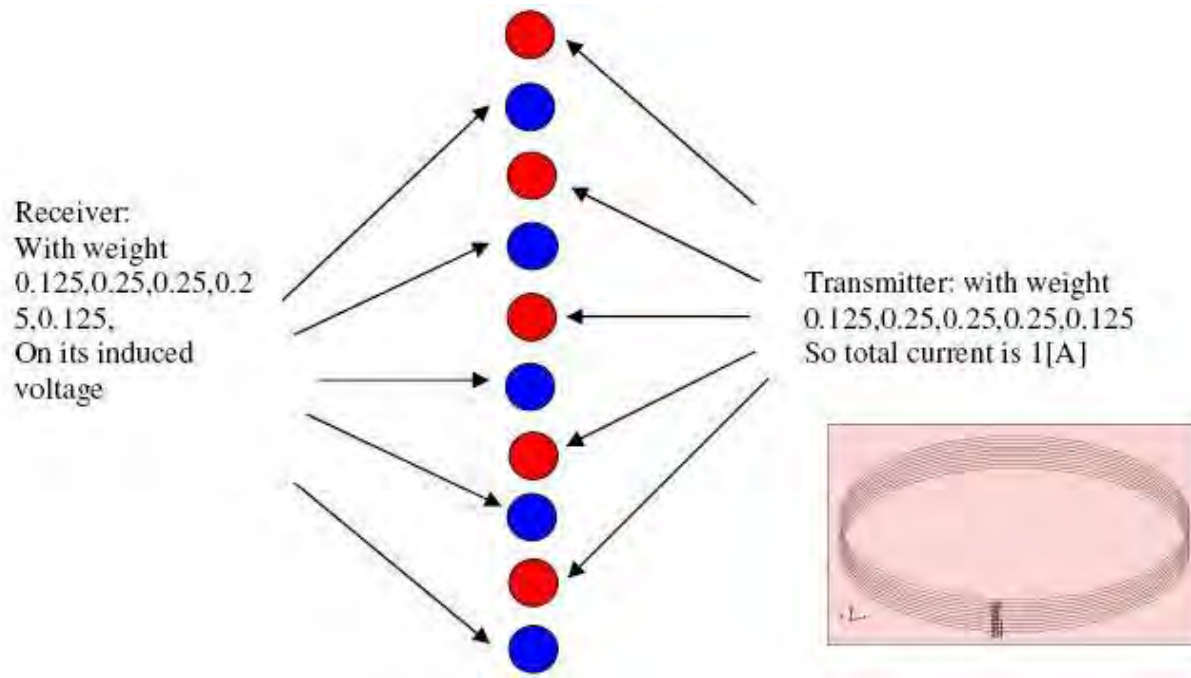Alternating Source and Field Configuration to accurately model self-impedance



	Z11 (@2MHz) in ohm
Model (without alternating)	3.61+i*169.39
Model (alternating)	3.56+i*107.29
Experimental results	3.54+i*101.34


Comparison with measurement with collar

$|Z|$ for unshielded ARC




Z phase for unshielded ARC

Absolute magnitude of antenna impedance

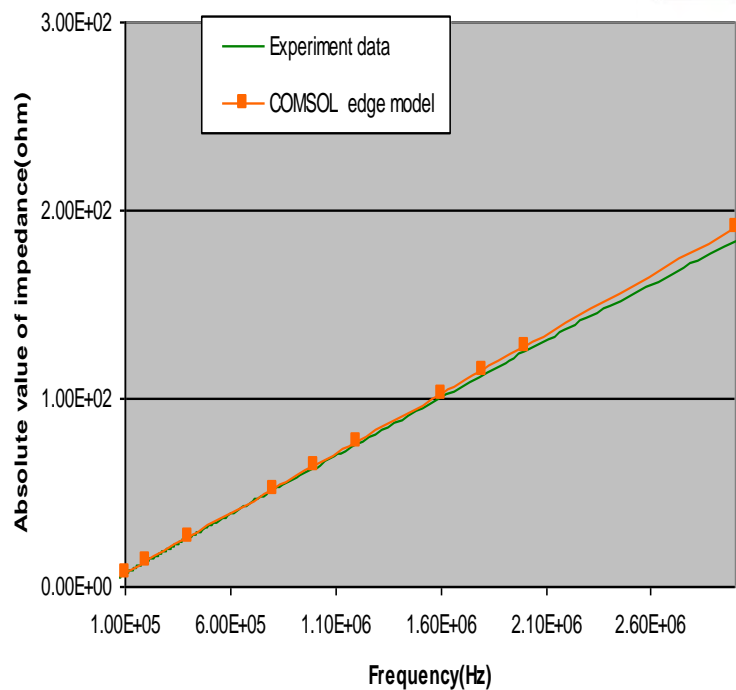


Phase angle of antenna impedance

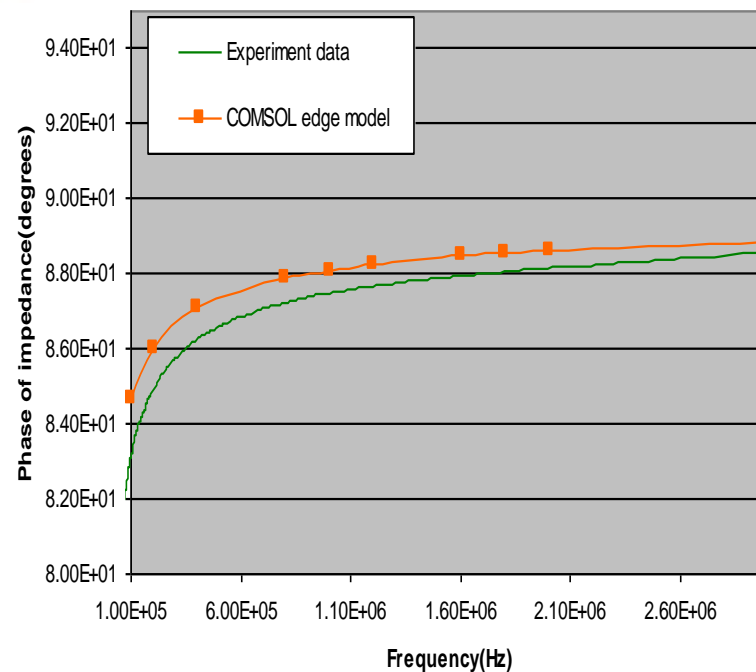


Comparison with measurement with collar and shield

$|Z|$ for shielded tool

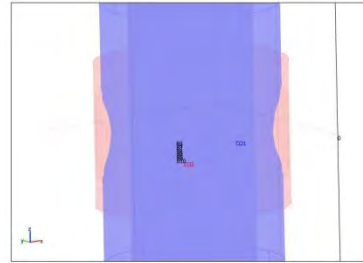


Z phase for shielded tool

absolute value of impedance

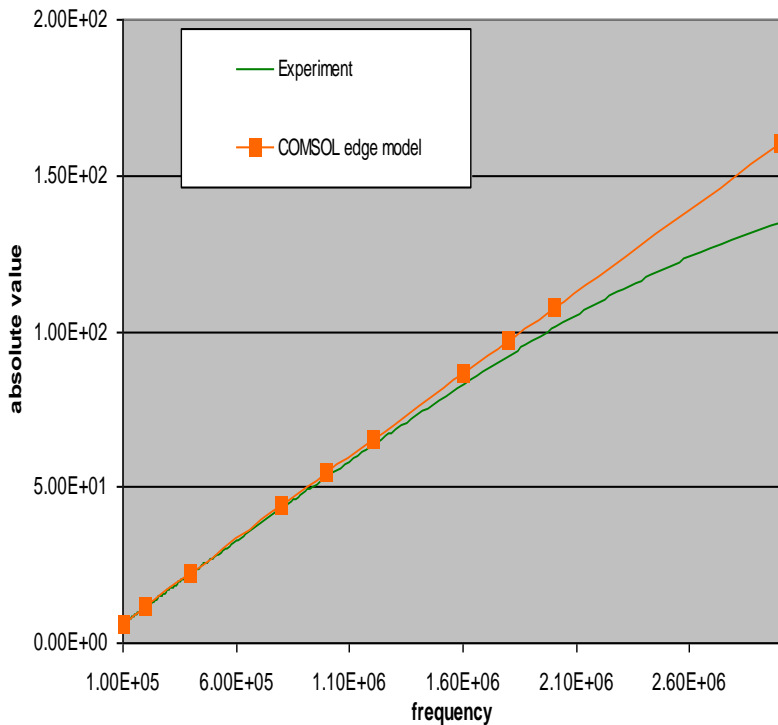

phase of impedance


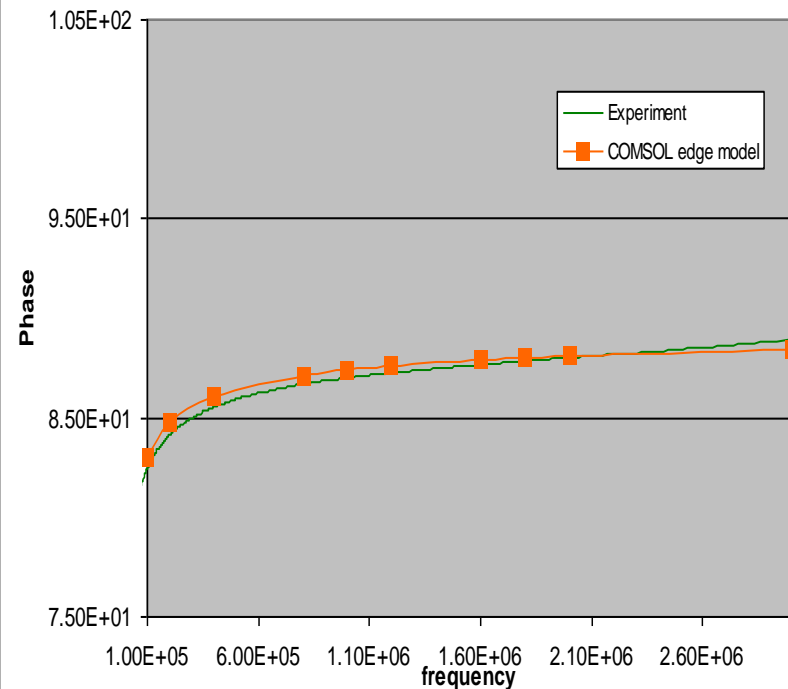


Superposition for modified Z




Freq. (MHz)	COMSOL Model		Analytical	
	Z_{COLLAR} (Ω)	Z_{AC} (air) (Ω)	Z_{AC} (air) (Ω)	
0.4	1.54 + i22.29	0.0032+i76.03	0.49+i77.28	
2.0	3.56 + i107.30	0.08+i378.78	1.03+i386.42	
Freq. (MHz)	Final	Measurement	$Z_{\text{collar}} - Z_{\text{MEAS}}$	
	Z_{TOTAL}^* (Ω)	Z_{MEAS} (Ω)	Mag. (Ω)	Phase ($^\circ$)
0.4	2.03 + i23.54 (23.63 \angle 85.08 $^\circ$)	22.43 \angle 85.54 $^\circ$	0.09	0.51
2.0	4.51 + i114.94 (115.03 \angle 87.75 $^\circ$)	101.4 \angle 88.02 $^\circ$	5.96	0.08

$$*Z_{\text{TOTAL}} = Z_{\text{COLLAR}} - Z_{\text{AIR_COMSOL}} + Z_{\text{AIR-ANALYTIC}}$$

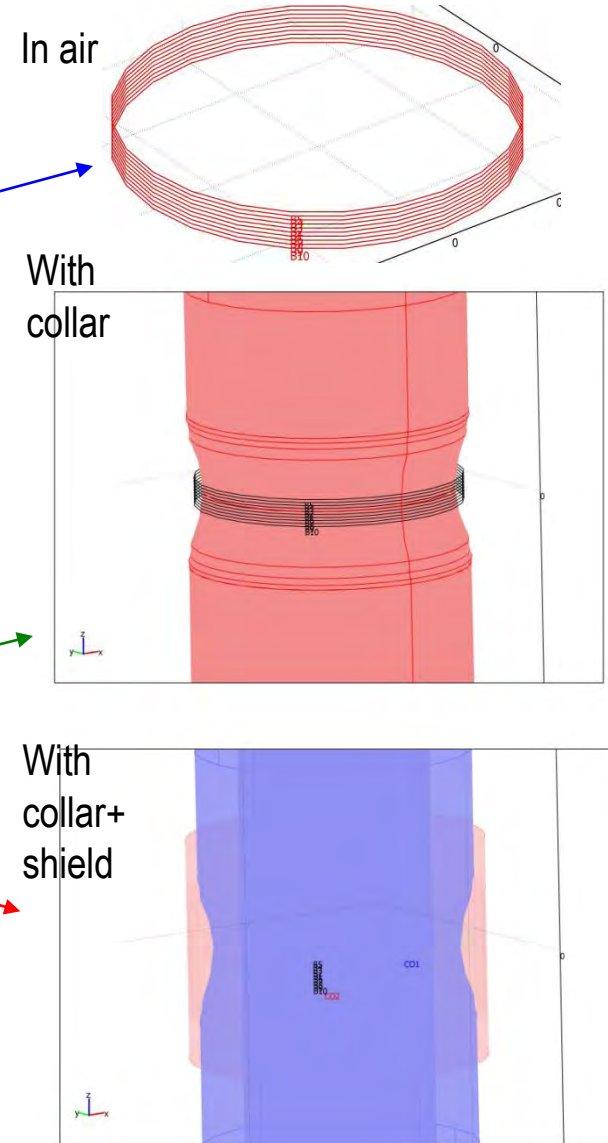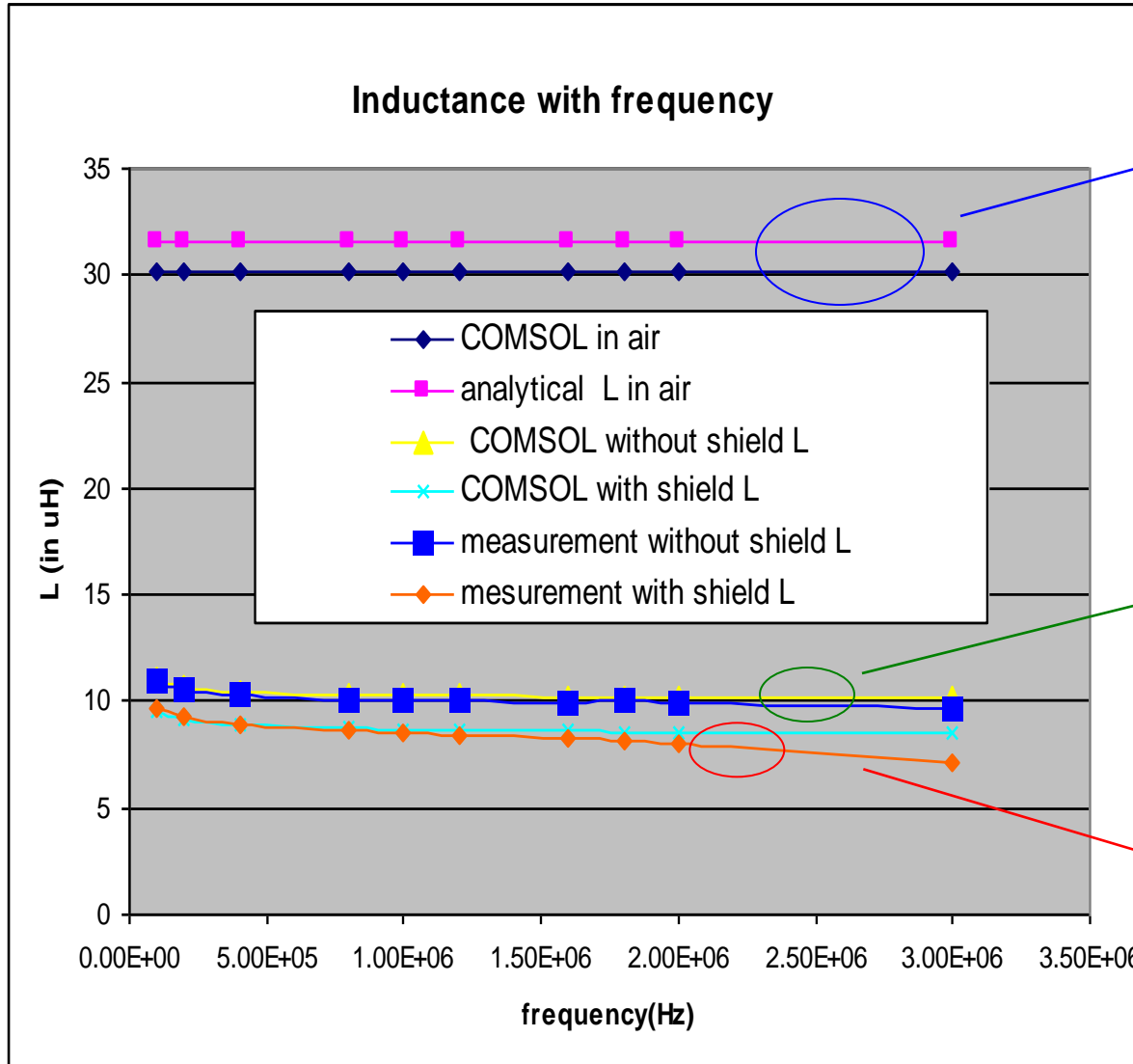Comparison with measurement: coil in air, with or without shield




Stray Capacitance C Modeling

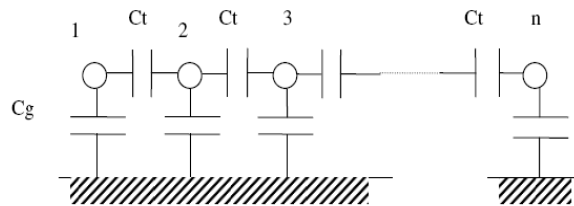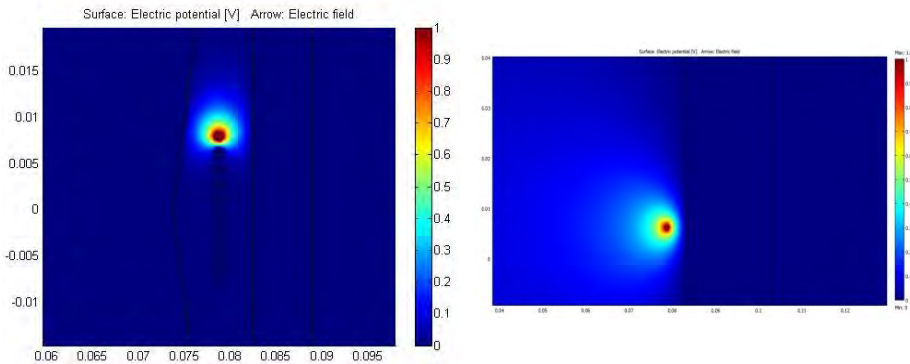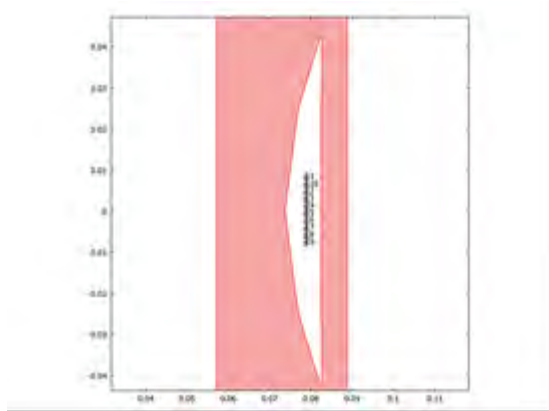



$$C = \begin{bmatrix} 0.0159 & 0.0075 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0; \\ 0.0075 & 0.0198 & 0.0073 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0; \\ 0 & 0.0073 & 0.0198 & 0.0073 & 0 \\ 0 & 0 & 0 & 0 & 0; \\ 0 & 0 & 0.0073 & 0.0198 & 0.0073 \\ 0 & 0 & 0 & 0 & 0; \\ 0 & 0 & 0 & 0.0073 & 0.0198 \\ 0.0073 & 0 & 0 & 0 & 0; \\ 0 & 0 & 0 & 0 & 0.0073 \\ 0.0198 & 0.0073 & 0 & 0 & 0; \\ 0 & 0 & 0 & 0 & 0 \\ 0.0073 & 0.0198 & 0.0073 & 0 & 0; \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0.0073 & 0.0199 & 0.0073 & 0; \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0.0073 & 0.0199 & 0.0075; \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0.0075 & 0.0161] \text{ nF};$$

Iterative Computation of Capacitance

N odd

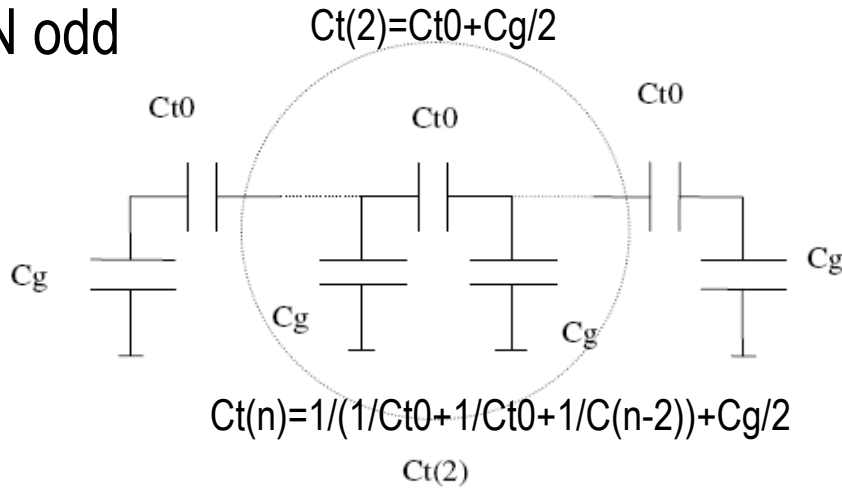

N even

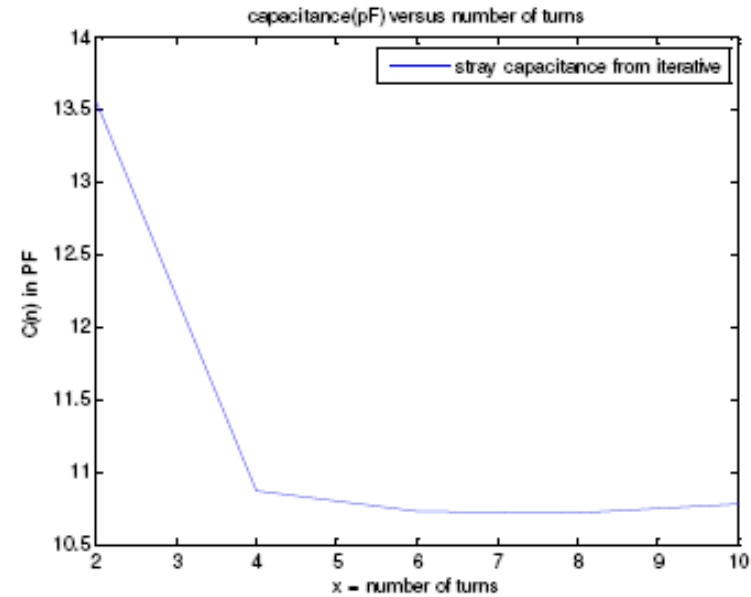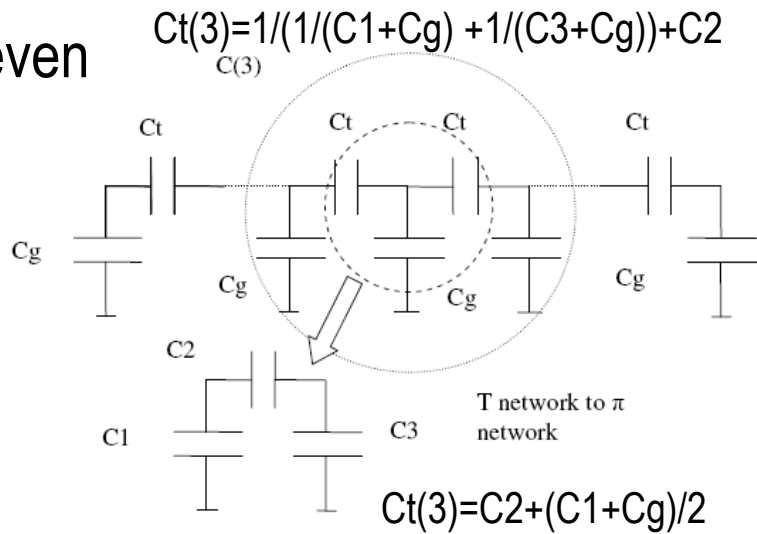


The overall capacitance in pF versus number of turns.


Converged $C = 10.78 \text{ pF}$ in air

To compute Resonant frequency and Z

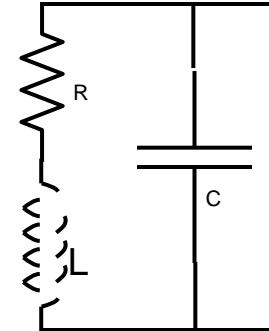
$$Z = 1 / \left(1 / (R + j\omega L) + j\omega \epsilon_r C \right)$$



impedance magnitude versus frequency

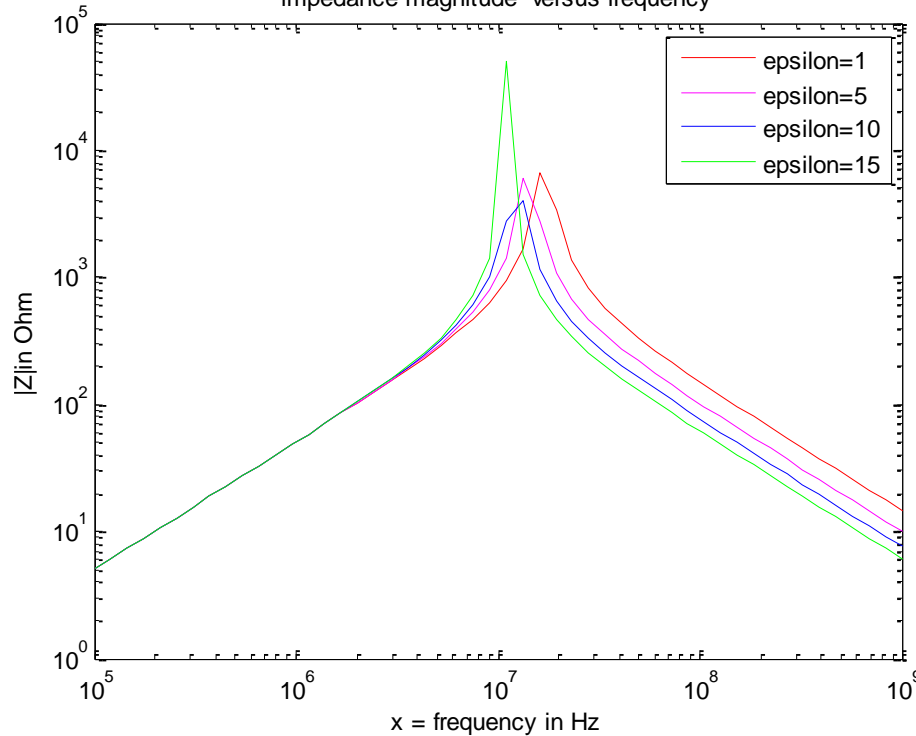

impedance phase versus frequency

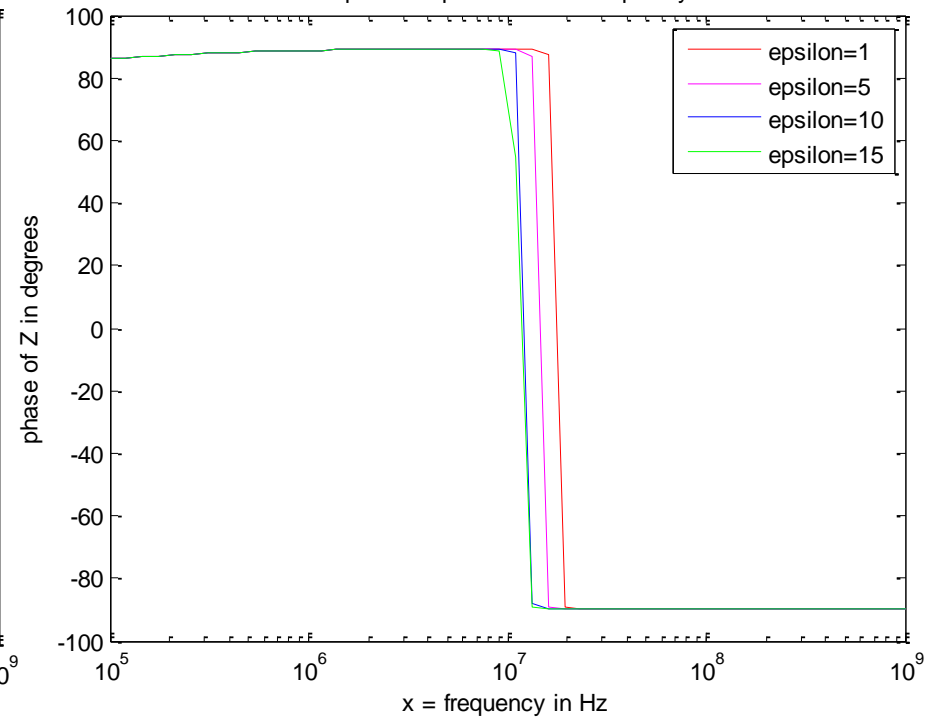




Conclusion

- An new approach of modeling the input impedance modeling is created using COMSOL, and it matches the measurement result well, it can model the high frequency thin wire coil accurately
- COMSOL can answer some challenging problems in electromagnetic sensor development

Thank you

Questions?

Array response

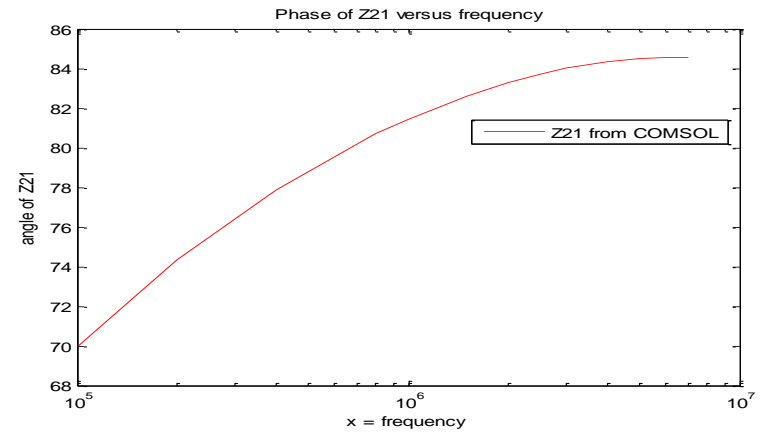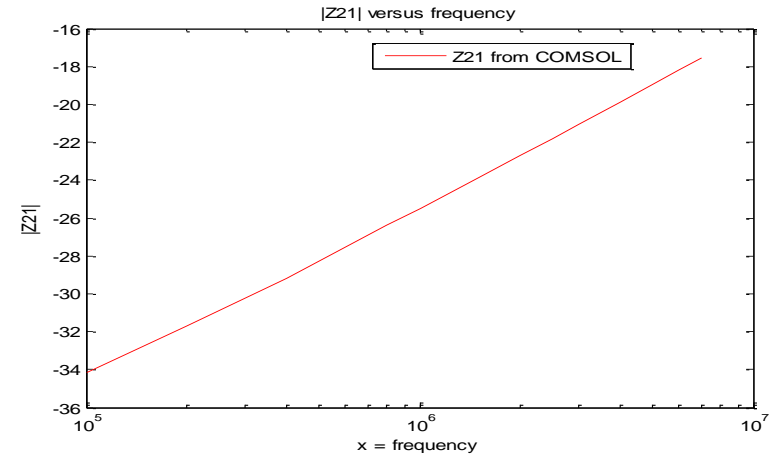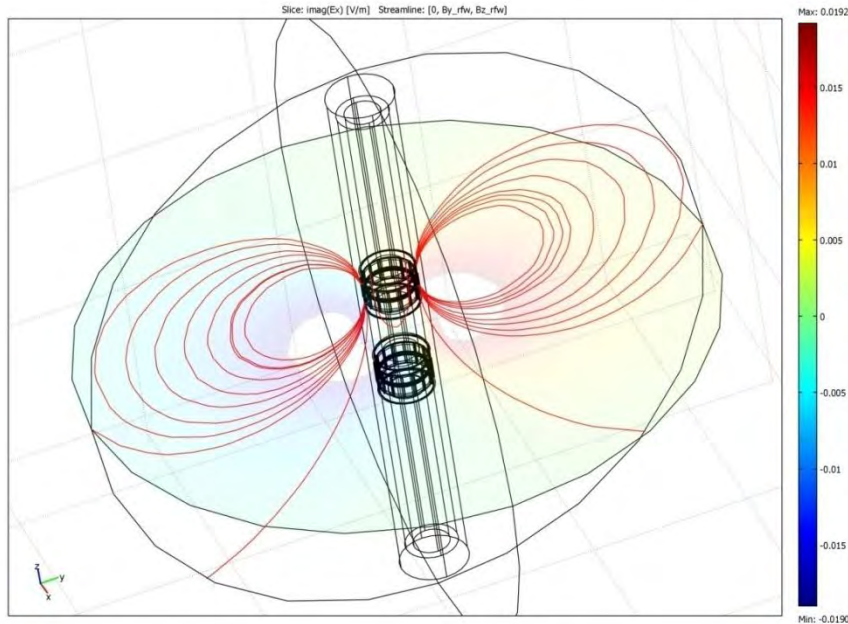

For antenna in air (no collar and shield), From Grover's book, $M=0.18\mu\text{H}$.

COMSOL $Z_{21}=1.637023\text{e-}4+i*0.453795$ ohm at 400k, $M=\text{imag}(Z_{21})/\omega=0.18056$ μH .

Model is validated by analytical result.

Z21 in 1 pair of TX and RX